

NAME: HRISHIKESH G KULKARNI

DATE: 02/06/2022

REG.NO.: 21BAI1660

BRANCH: BTECH - CSE AND SPEC IN AI/ML – VITCHENNAI

BECE101P_SLOT-L5+L6_EXPERIMENT – 11

FACULTY: PROF. SASITHRADEVI MA'AM

RC Phase Shift Oscillator

AIM: To study, understand and simulate the RC Phase shift oscillator using LT-spice.

SOFTWARE REQUIRED: **LT-Spice**


Apparatus required: In LT-Spice we use wires, grounding cables, resistors, capacitors, Npn – transistor and voltage source.

Theory:


RC phase-shift oscillators use resistor-capacitor (RC) network (Figure 1) to provide the phase-shift required by the feedback signal. They have excellent frequency stability and can yield a pure sine wave for a wide range of loads.

PROCEDURE:

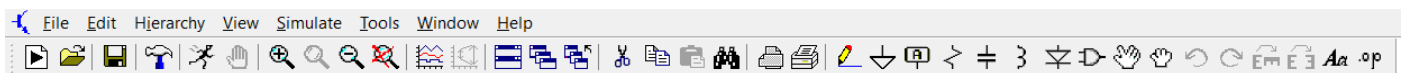
1. Click on the components (component library) button on the toolbar, and then using the components draw the circuit exactly as shown in circuit diagram (later shown) using npn-transistor, resistors, capacitors, grounding, wires and voltage sources.



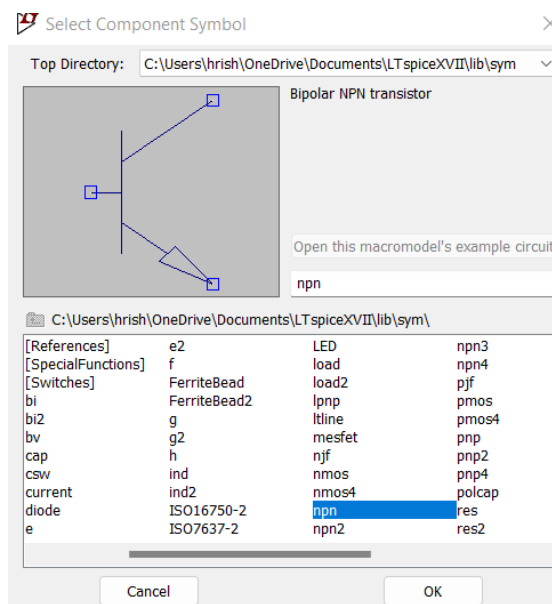
2. In the component library choose the npn transistor and connect it in the circuit as shown in the circuit diagram.



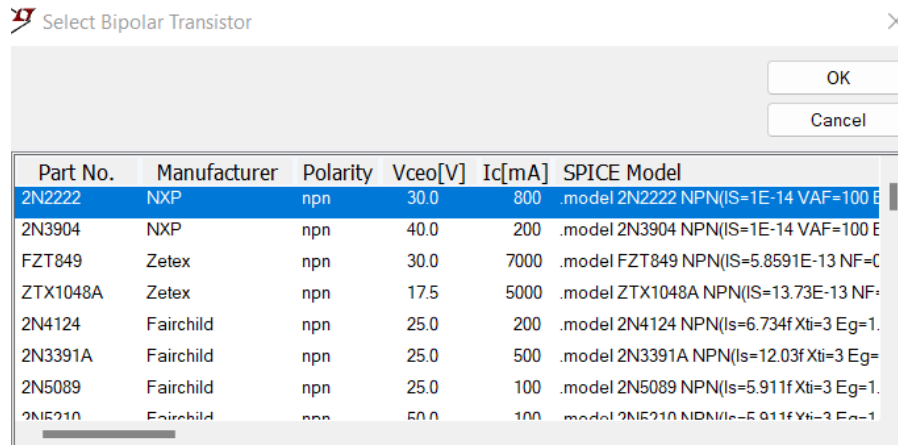- Now right click the transistor and click pick new diode. choose the npn transistor – 2N2222 as shown in the circuit diagram.



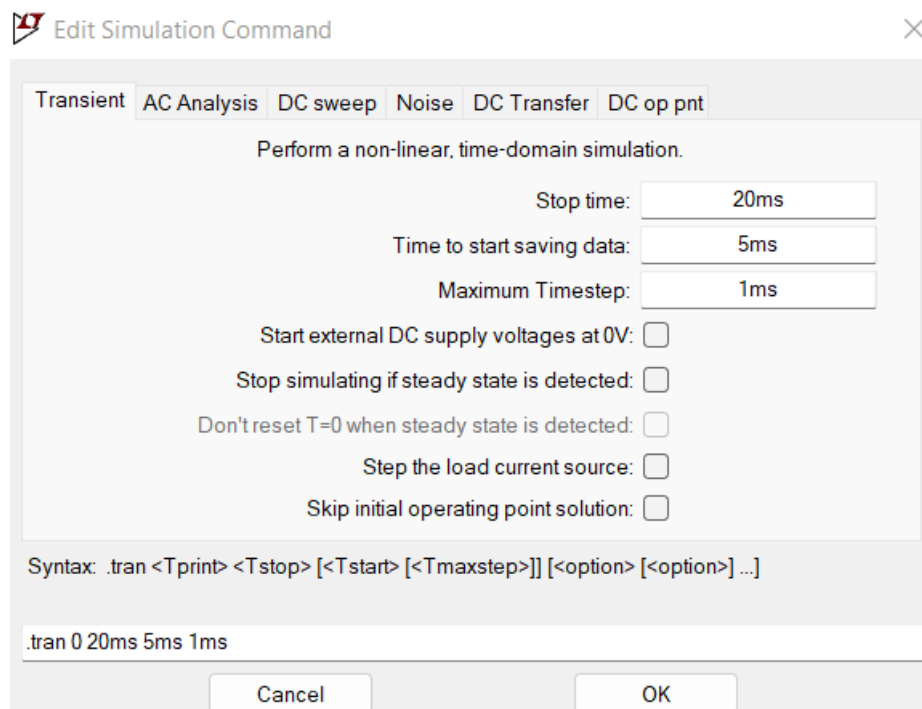
- Give the value for resistors, capacitors and voltage source as shown in the circuit diagram. Also make the connection properly. Do not forget to add grounding.
- Now, under simulation → click on edit simulation command and then under transient give the parameters as shown below.




- Next, under simulation, click on Run (or click on run symbol).
- Now, when graph appears, left click on the right-hand side terminal of the C4(Vnc_01) capacitor and this would give us the RC Phase shift Oscillator OUTPUT.

CIRCUIT DIAGRAM

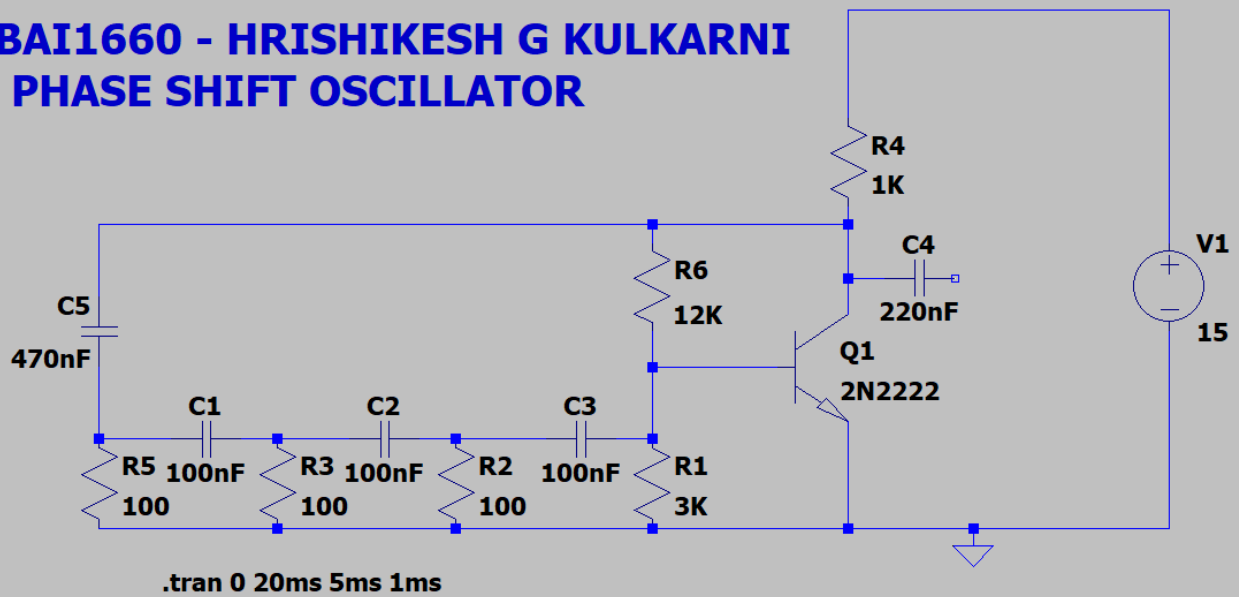21BAI1660 - HRISHIKESH G KULKARNI RC PHASE SHIFT OSCILLATOR



OUTPUT

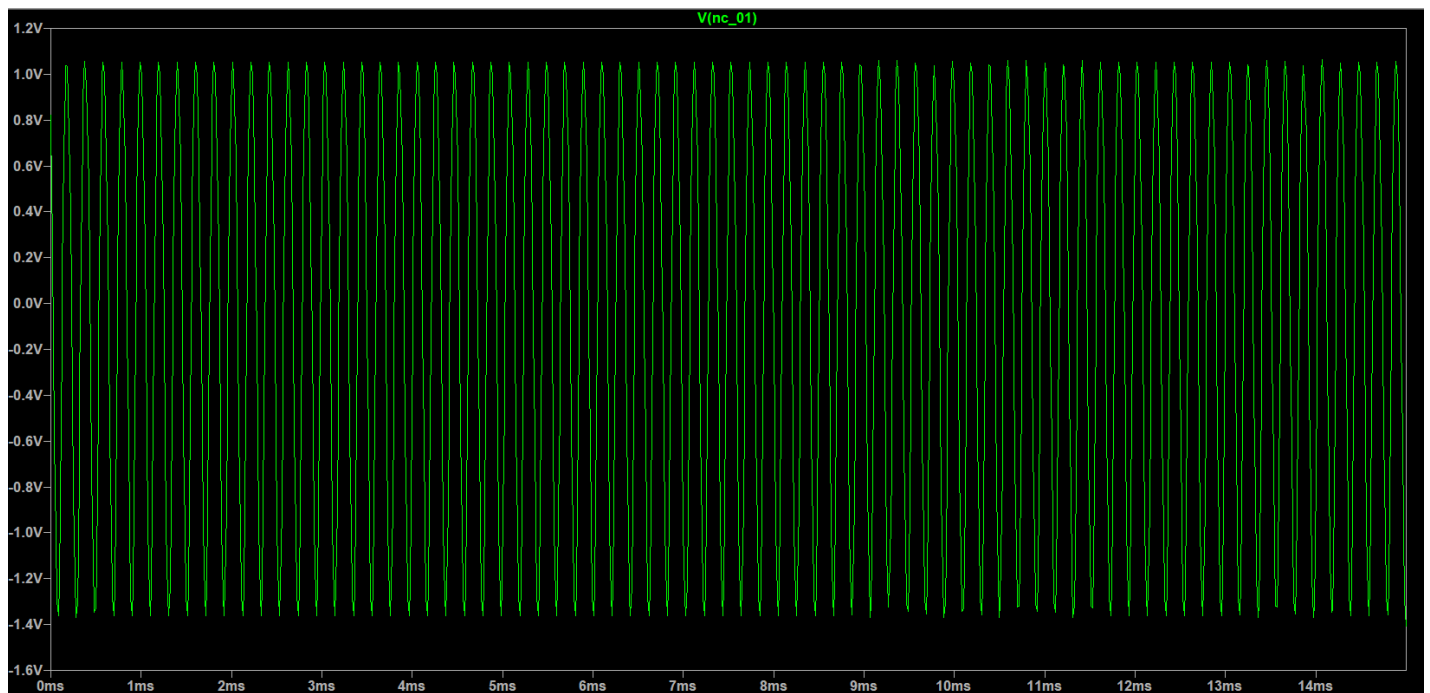

Result and Inference

From the LT-spice simulation, we were able to study, understand, observed and verify the RC Phase shift oscillator output.

=====THE-END=====